
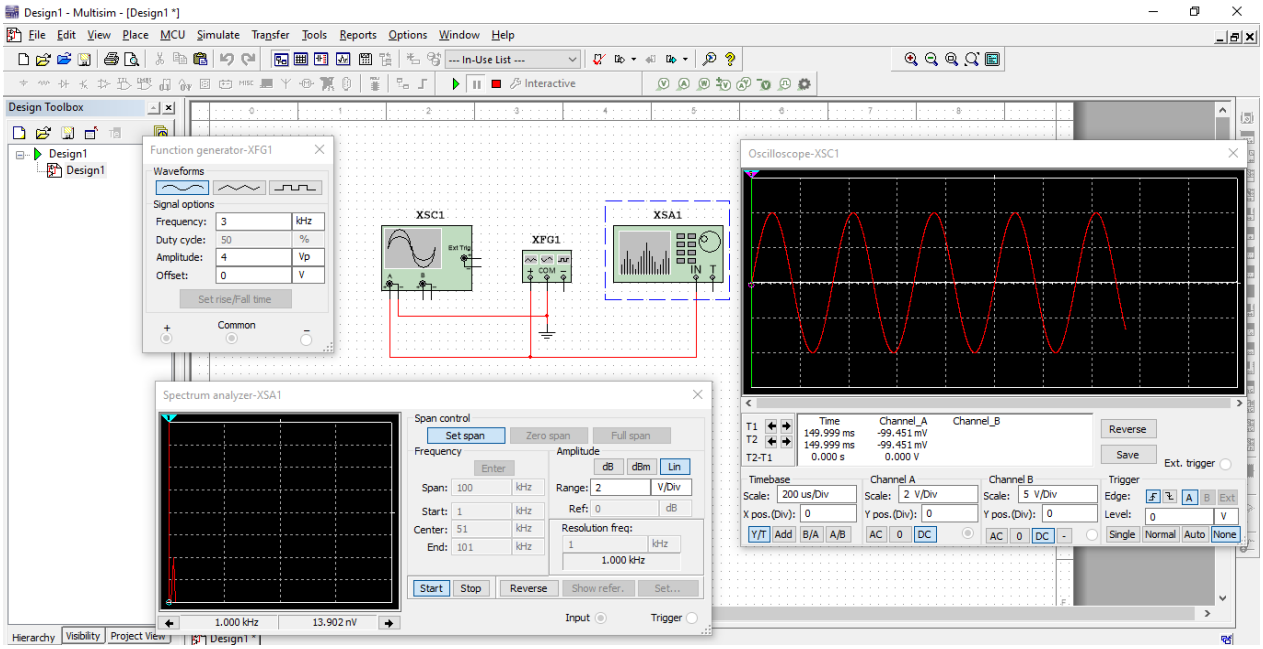
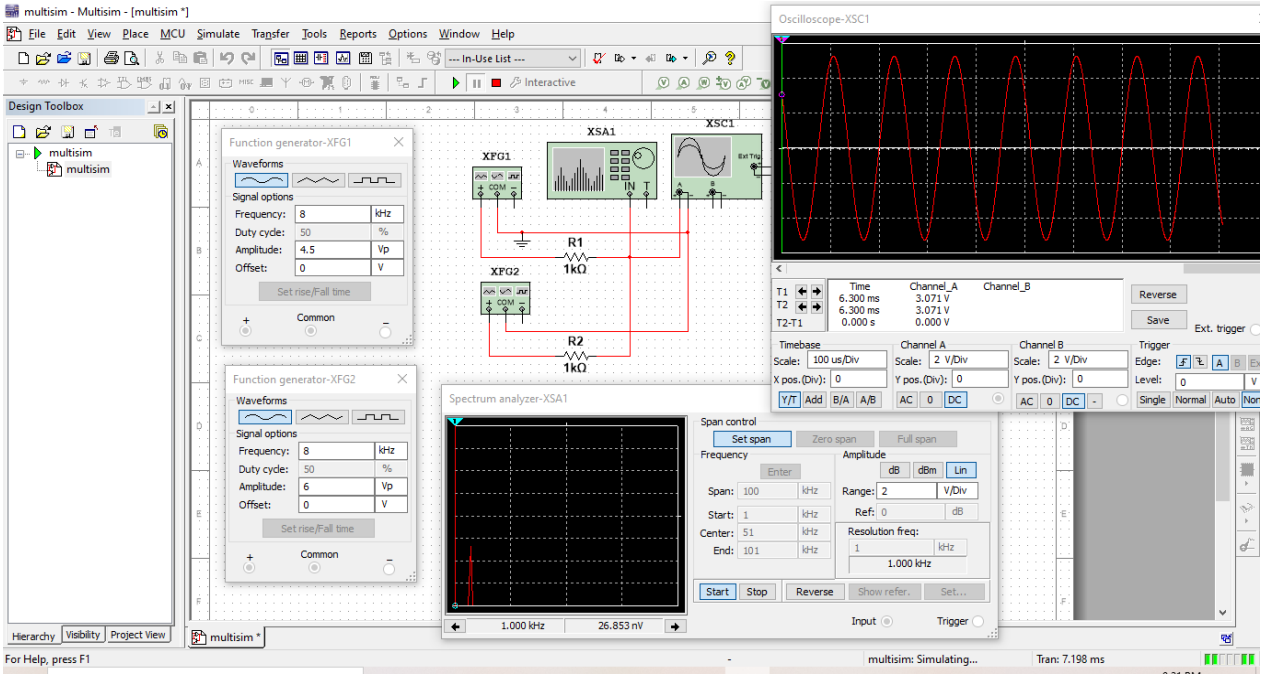
# Latihan Oscilloscope dan Spectrum Analyser Menggunakan Aplikasi Multisim




Gambar no. 1

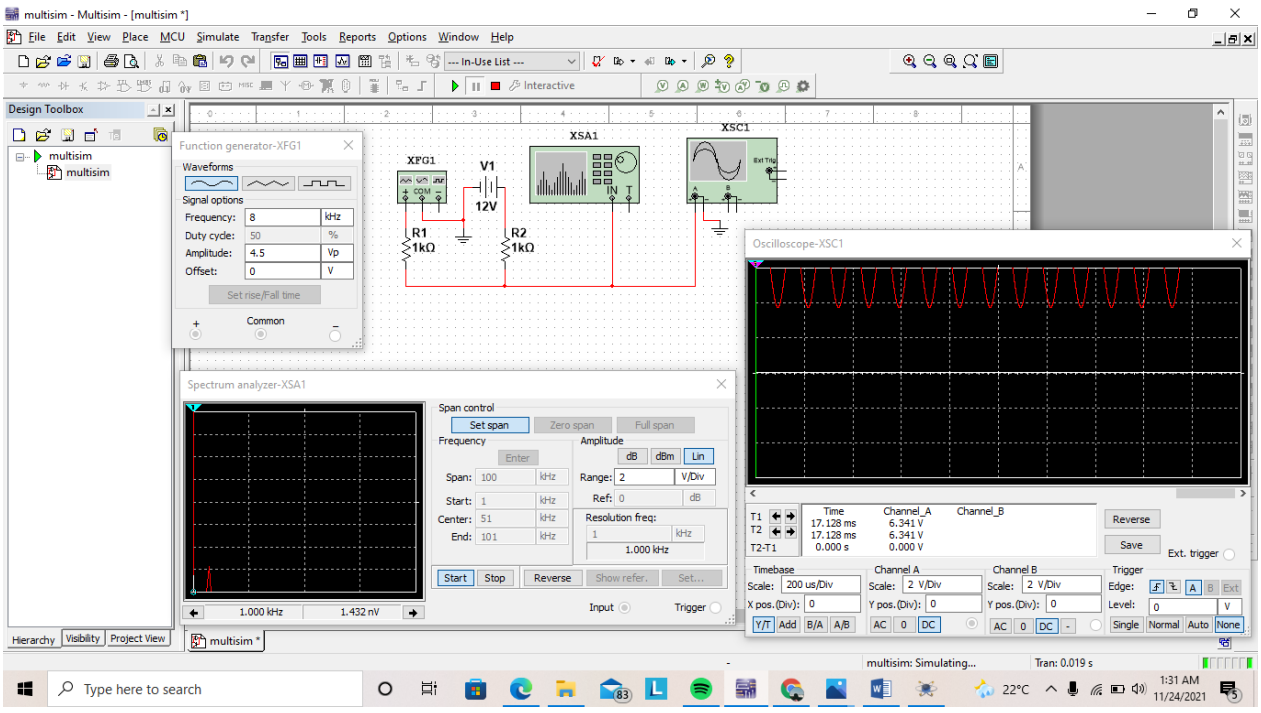



Gambar no.2



multisim - Multisim - [multisim *]
File Edit View Place MCU Simulate Transfer Tools Reports Options Window Help
Design Toolbox
multisim
multisim
Function generator-XFG1
Waveforms
Signal options
Frequency: 8 kHz
Duty cycle: 50 %
Amplitude: 4.5 Vp
Offset: 0 V
Set rise/Fall time
Common
XFG1
V1
12V
R1
1kΩ
R2
1kΩ
XSA1
XSC1
Oscilloscope-XSC1
Time Channel_A Channel_B
T1 17.128 ms 6.341 V
T2 17.128 ms 6.341 V
T2-T1 0.000 s 0.000 V
Reverse
Save
Ext. trigger
Timebase
Scale: 200 us/Div
X pos.(Div): 0
Channel A
Scale: 2 V/Div
Y pos.(Div): 0
Channel B
Scale: 2 V/Div
Y pos.(Div): 0
Trigger
Edge:
Level: 0 V
Single Normal Auto None
Spectrum analyzer-XSA1
Span control
Set span Zero span Full span
Frequency
Span: 100 kHz
Start: 1 kHz
Center: 51 kHz
End: 101 kHz
Amplitude
Range: 2 V/Div
Ref: 0 dB
Resolution freq: 1 kHz
1.000 kHz
Start Stop Reverse Show refer. Set...
Input Trigger
1.000 kHz 1.432 nV
Hierarchy Visibility Project View
multisim *
multisim: Simulating...
Tran: 0.019 s
Type here to search
22°C
1:31 AM
11/24/2021

Gambar no.3

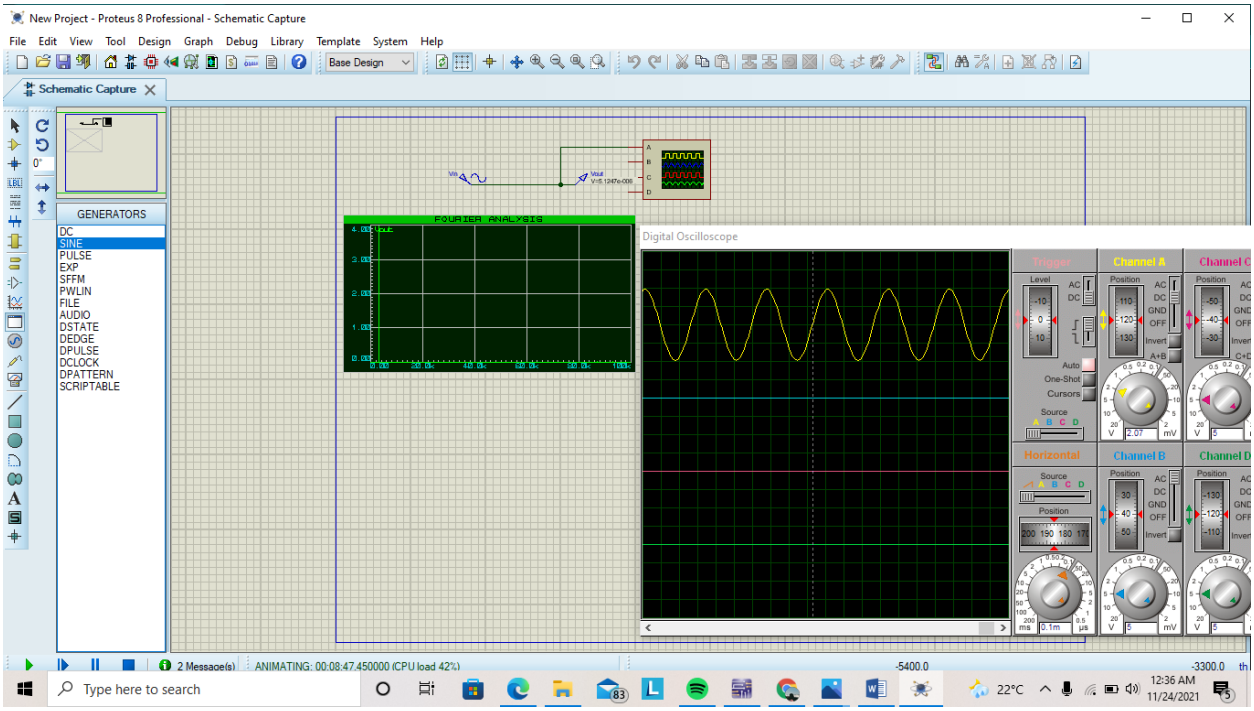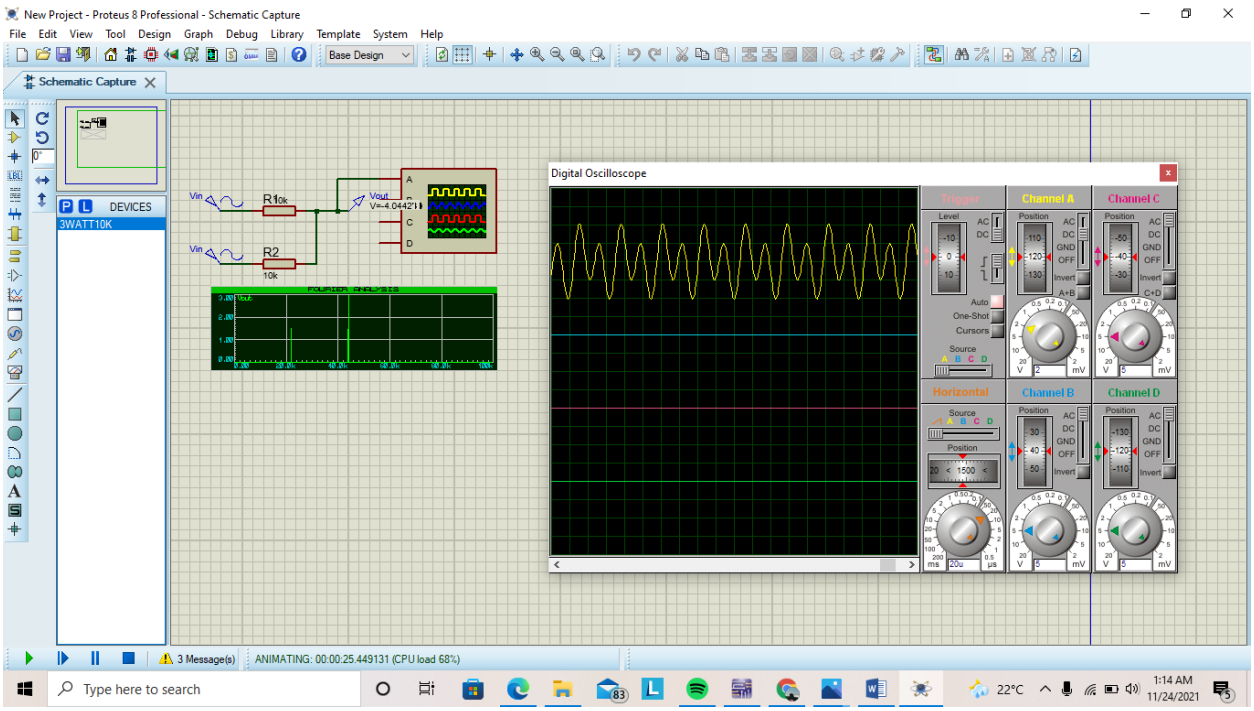
# Latihan Oscilloscope dan Spectrum Analyser Menggunakan Aplikasi Proteus




Gambar no.1




Gambar no.2

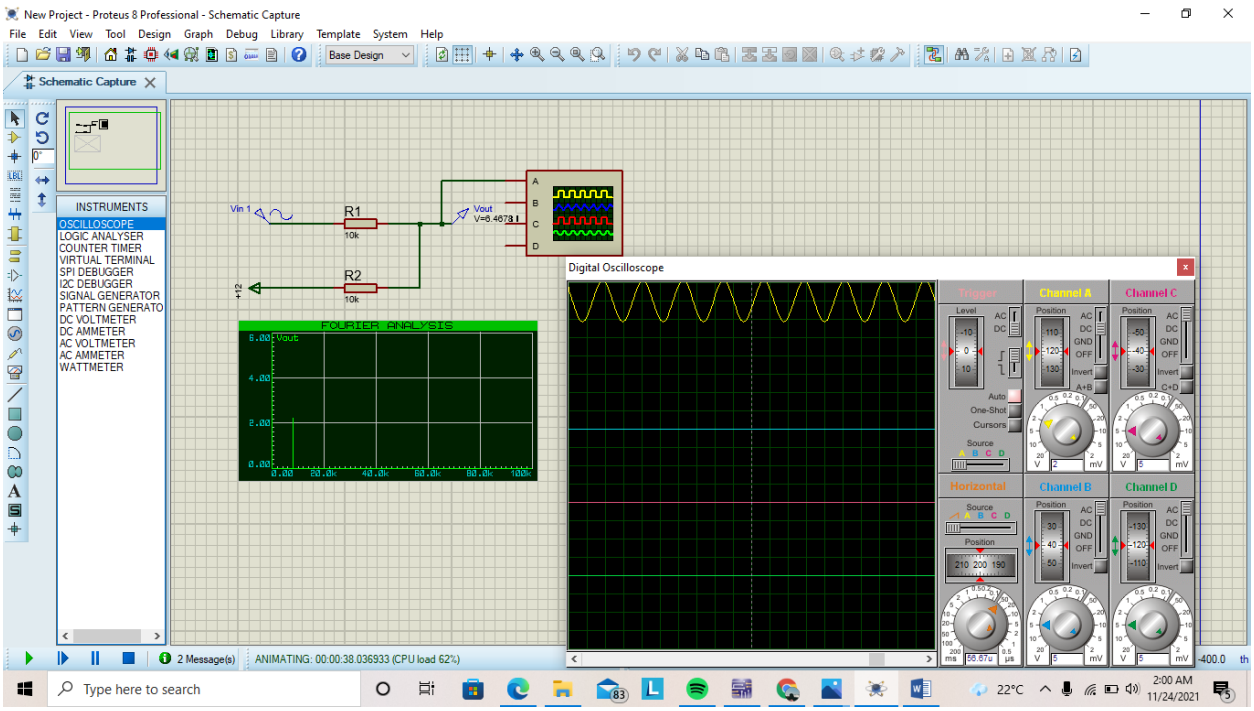


Gambar no.3