
Livewire - Professional Edition - [Tugas 1.lvw]

File Edit View Insert Tools Window Help

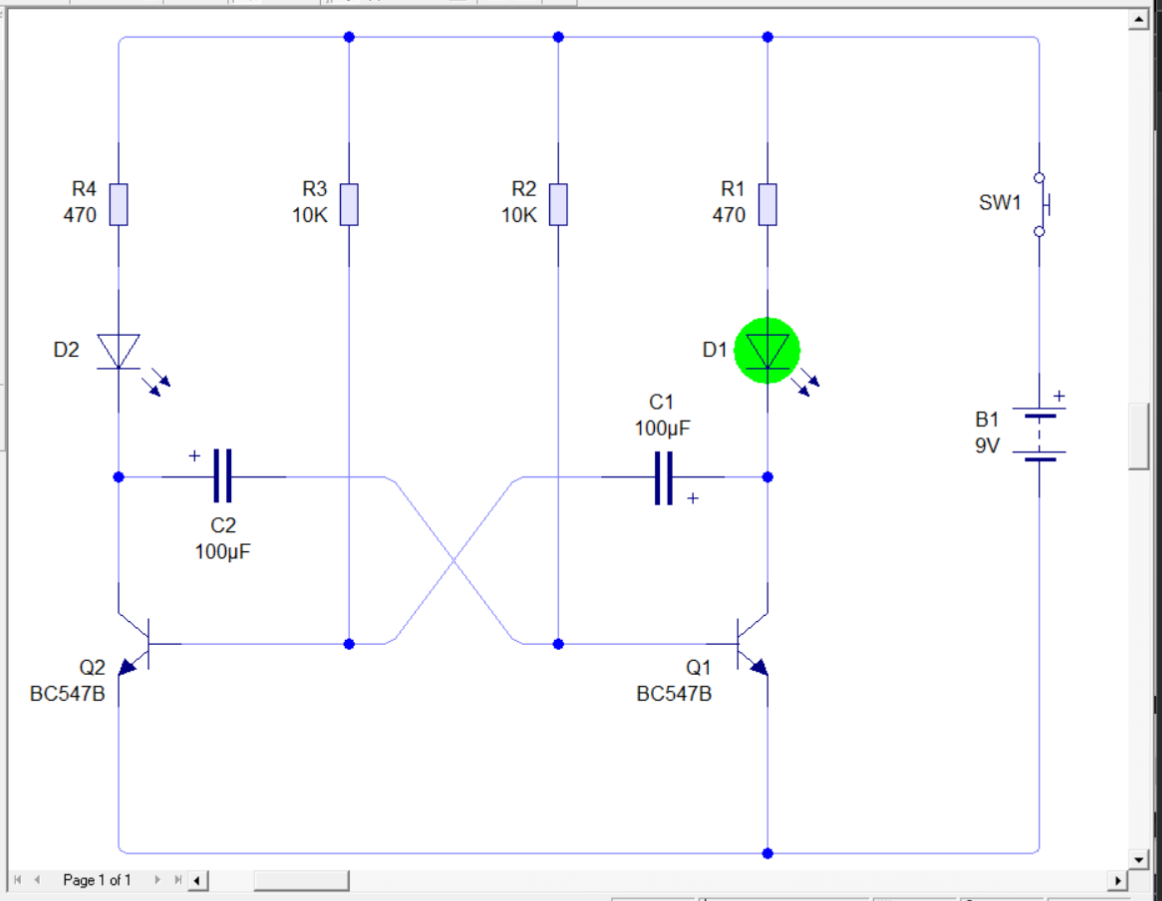


Page 1 of 1

Press F1 for help | Time: 11.807 s | -294.64, 71.12 mm | 0.1 in | 175% | Ready

drive.google.com/file/d/1wUkECJbA9olp...

Tugas-8. ... atik.pdf | Buka...

berikut menggunakan Livewire

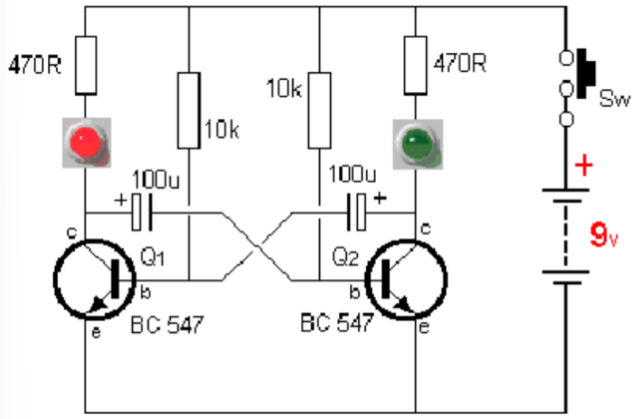

buat skema dari skema yang suda

Halaman 2 / 4

30°C Mostly cloudy

Search

3:53 PM 10/23/2023

Livewire - Professional Edition - [Tugas 1.lvw]

File Edit View Insert Tools Window Help

Normal Voltage Levels Current Flow Logic Levels More

R4 470
R3 10K
R2 10K
R1 470
SW1
D2
D1
C1 100µF
B1 9V
C2 100µF
Q2 BC547B
Q1 BC547B


Page 1 of 1

Press F1 for help Time: 20.350 s -294.64, 71.12 mm 0.1 in 175% Ready

drive.google.com/file/d/1wUkECJbA9olp...

Tugas-8. ... atik.pdf Buka...

berikut menggunakan Livewire

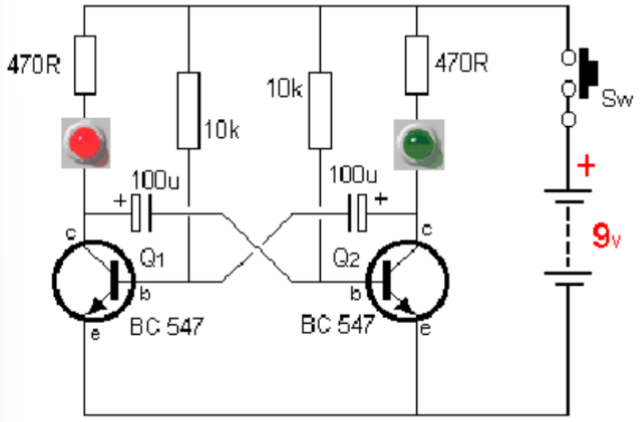

buat skema dari skema yang suda

Halaman 2 / 4

30°C Mostly cloudy


Search

3:53 PM 10/23/2023

Livewire - Professional Edition - [Tugas 2.lvw *]

File Edit View Insert Tools Window Help

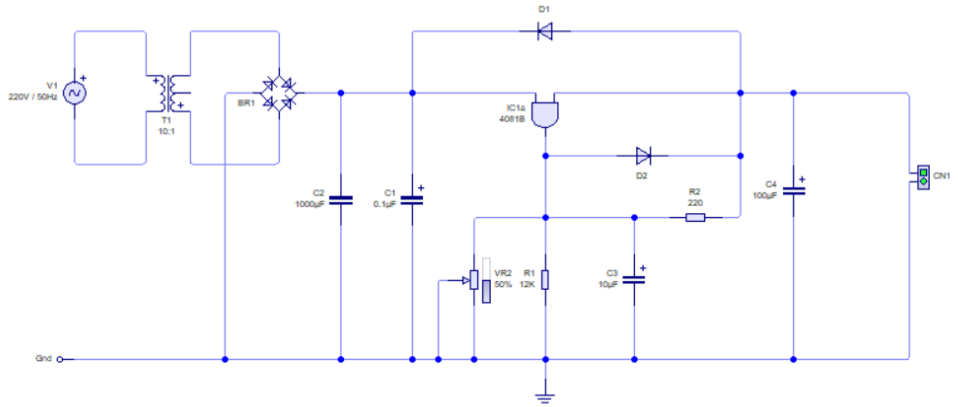Normal Voltage Levels Current Flow Logic Levels More



Page 1 of 1

Press F1 for help | Time: 3.814 s | 287.02, 33.02 mm | 0.1 in | 75% | Ready

GAMBA | Livewire | Tugas-B


drive.google.com/file/d/1wUkECJbA9oIpDnPz...

Tuga ... .pdf | Buka...

an membuat skema dari skema yang sudah ada

2

h skema berikut menggunakan Livewire

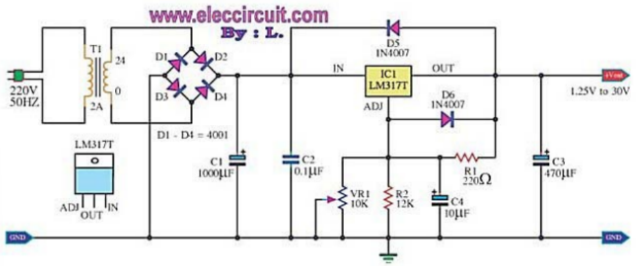

an membuat skema dari Diagram Pictorial

3

ah Diagram Skema

Halaman 3 / 4

30°C
Mostly cloudy


Search

3:37 PM
10/23/2023

Livewire - Professional Edition - [Tugas 3.lvw *]

File Edit View Insert Tools Window Help

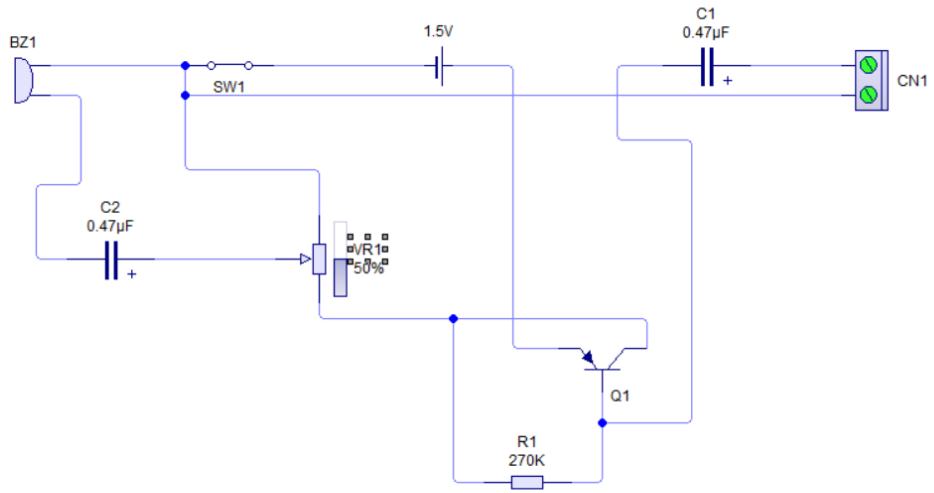Normal Voltage Levels Current Flow Logic Levels More



Page 1 of 1


Press F1 for help | Time: 103.321 s | 223.52, 124.46 mm | 0.1 in | 125% | Ready

GAMB | Livewi | Tugas

drive.google.com/file/d/1wUkECJbA9olp...

Tugas-8. ... atik.pdf | Buka...

t skema dari Diagram Pictorial

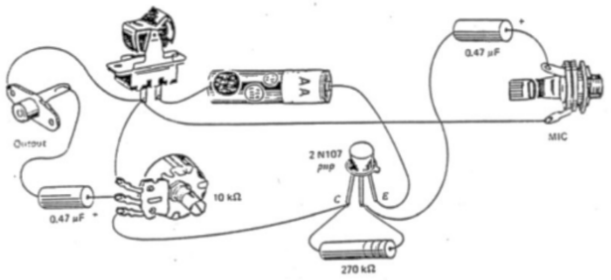

Microphone preamplifier circuit

Halaman 4 / 4

30°C Mostly cloudy

Search

4:01 PM 10/23/2023